

You may use a calculator, straight edge, and compass on this exam. No other tools, notes, or textbooks are permitted. Below is a list of relevant formulas which you may or may not need for the exam. These are sufficient to solve all the problems.

Physical Constants

$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

$c = 3.0 \times 10^8 \text{ m/s}$

Transmission Line Theory

$-\frac{\partial \tilde{V}(z)}{\partial z} = (R' + j\omega L') \tilde{I}(z)$

$-\frac{\partial \tilde{I}(z)}{\partial z} = (G' + j\omega C') \tilde{V}(z)$

$\gamma = \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')}$

$\tilde{Z}_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$

$\lambda = 2\pi / \beta$



Lossless lines

$\gamma = 0 + j\beta = j\omega \sqrt{L' \cdot C'}$


$Z_0 = \sqrt{L'/C'}$

Input Impedance

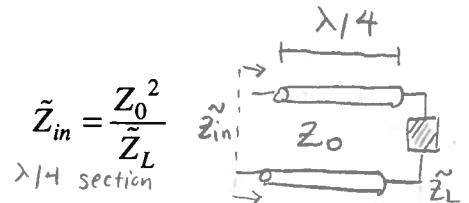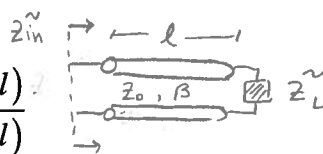
general case $\tilde{Z}_{in}(-l) = Z_0 \times \frac{\tilde{Z}_L + j \cdot Z_0 \cdot \tan(\beta l)}{Z_0 + j \cdot \tilde{Z}_L \cdot \tan(\beta l)}$



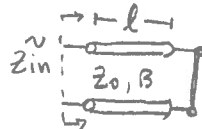Short load $\tilde{Z}_{in}(-l) = j \cdot Z_0 \cdot \tan(\beta l)$



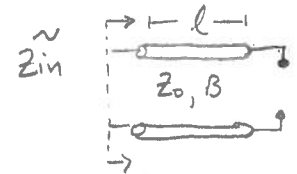open load $\tilde{Z}_{in}(-l) = -j \cdot Z_0 \cdot \cot(\beta l)$




Voltage Reflection Coefficients

$\tilde{\Gamma}_L = \frac{\tilde{Z}_L - Z_0}{\tilde{Z}_L + Z_0}$

$\Gamma_G = \frac{R_G - Z_0}{R_G + Z_0}$

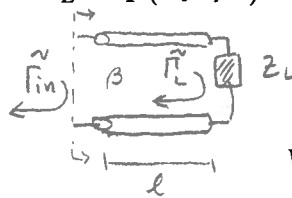
$\tilde{\Gamma}_{in}(-l) = \frac{\tilde{Z}_{in}(-l) - Z_0}{\tilde{Z}_{in}(-l) + Z_0} = \tilde{\Gamma}_L \cdot \exp(-j2\beta l)$



Transient Analysis



$u_p = \frac{\Delta z}{\Delta t} = \frac{c}{\sqrt{\epsilon_r}}$

$V_1^+ = V_g \frac{Z_0}{Z_0 + R_G}$

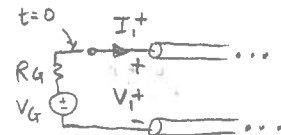

$V_n^- = V_n^+ \cdot \Gamma_L \text{ for } n = (1..∞)$

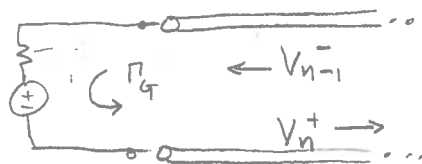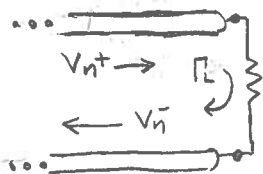$V_n^+ = V_{n-1}^- \cdot \Gamma_G \text{ for } n = (2..∞)$



$I_n^+ = V_n^+ / Z_0$

$I_n^- = -V_n^- / Z_0$