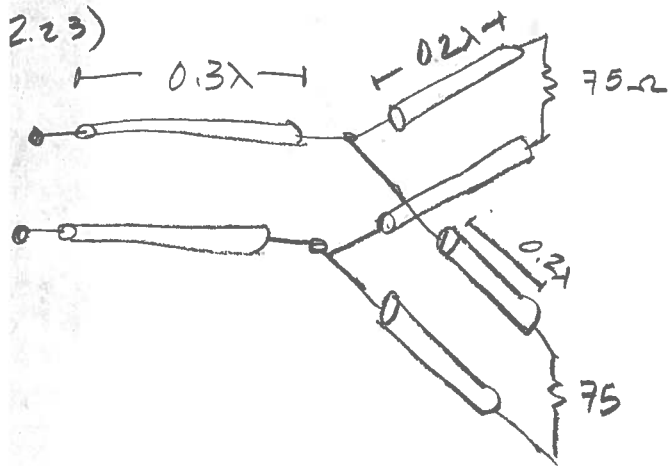


Ryan Chilton
ECE 311 - HW#3 Solutions




(a) Find the input impedance of one antenna at the Y-junction:

$$\tilde{Z}_i = \frac{\tilde{Z}_L + jZ_0 \tan(\beta l)}{Z_0 + j\tilde{Z}_L \tan(\beta l)} \quad \begin{cases} Z_L = 75\Omega \\ Z_0 = 50\Omega \\ \beta l = \frac{2\pi}{\lambda} \cdot 0.2 \\ = 72 \text{ degrees} \end{cases}$$

$$\tilde{Z}_i = \frac{75 + j50 \cdot \tan(72^\circ)}{50 + j75 \cdot \tan(72^\circ)} \cdot Z_0 = \underline{35.2 - j8.6\Omega}$$

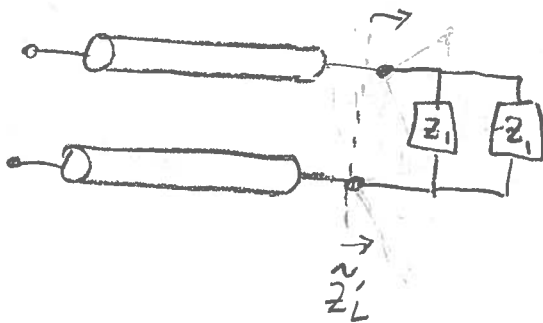
(b) Combine the two antennas impedances in parallel to find the total impedance at the Y-junction:



$$\tilde{Z}_L' = (\tilde{Z}_i \parallel \tilde{Z}_i) = \frac{\tilde{Z}_i \cdot \tilde{Z}_i}{\tilde{Z}_i + \tilde{Z}_i} = \frac{1}{2} \tilde{Z}_i$$

$$\tilde{Z}_L' = (17.6 - j4.3)\Omega$$

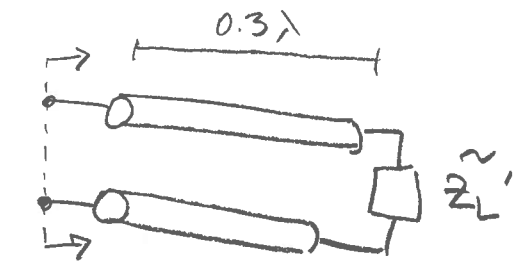(c) Transform this impedance all the way back to the feed point




$$\tilde{Z}_{in} = \frac{\tilde{Z}_L' + jZ_0 \tan(\beta l)}{Z_0 + j\tilde{Z}_L' \tan(\beta l)} \cdot Z_0 \quad \begin{cases} \tilde{Z}_L' = 17.6 - j4.3 \\ Z_0 = 50 \\ \beta l = \frac{2\pi}{\lambda} \cdot 0.3 \\ = 108^\circ \end{cases}$$

$$\tilde{Z}_{in} = \frac{(17.6 - j4.3) + j50 \tan(108^\circ)}{50 + j(17.6 - j4.3) \tan(108^\circ)} \cdot Z_0$$

$$= \underline{(107.6 - j56.7)\Omega}$$

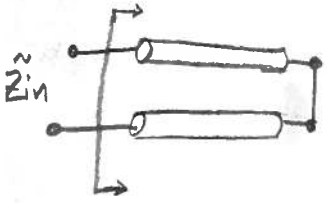
(2.24) Design a shorted transmission line to realize a reactance of $+j40\Omega$. Parameters: $f=300\text{ MHz}$, $Z_0=50\Omega$, $n_p=0.75c_0$



$$\tilde{Z}_{in} = j \cdot Z_0 \cdot \tan(\beta l) = +j40\Omega$$

$$\tan(\beta l) = \frac{40\Omega}{50\Omega} = 0.8$$

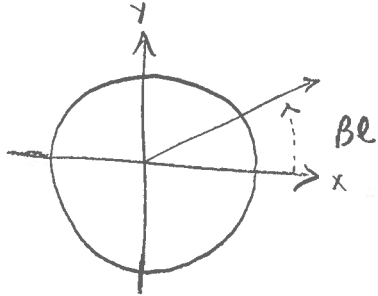Draw this on a circle to work out the trig:



Sketch shortest possible βl such that $\tan(\beta l) = 0.8$ and βl is still positive

$$\beta l = 38.66^\circ$$

Use phase velocity to find β

$$u_p = \frac{\omega}{\beta} \quad \rightarrow \quad \text{solve for } \beta \quad \beta = \frac{\omega}{u_p} = \frac{300 \times 10^6 \times 2\pi \text{ rad/sec}}{0.75 \times 3 \times 10^8 \text{ m/s}}$$


$$\beta = 8.378 \text{ rad/m}$$

Put it all together to find l :


$$\beta l = 38.66^\circ = 0.675 \text{ rad}$$

$$\therefore l = \frac{0.675 \text{ rad}}{\beta} = \frac{0.675 \text{ rad}}{8.378 \text{ rad/m}} \approx 0.08 \text{ m} \\ = 8 \text{ cm}$$

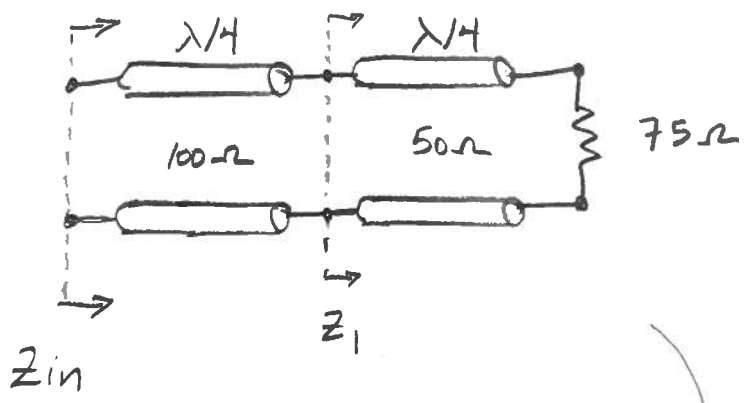(2.27) Cascaded quarter wave transformers ... use equation 2.77, twice.


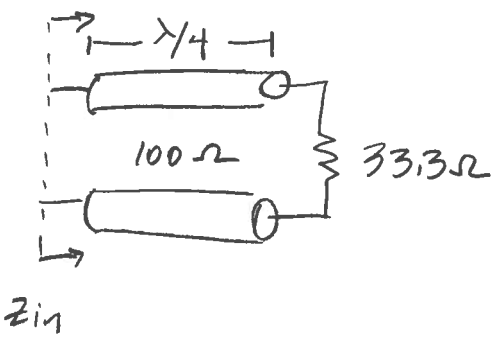
$$Z_1 = \frac{(50\ \Omega)^2}{75\ \Omega} = 33.3\ \Omega$$



$$Z_{in} = \frac{(100\ \Omega)^2}{33.3\ \Omega} = 300\ \Omega$$

(2.35)

(a) $\tilde{z}_L = 3z_0$
 $\tilde{h}_L = 3 + j0$
 $\dots \tilde{\Gamma} \approx 0.5 \angle 0^\circ$

The Complete Smith Chart

Black Magic Design



(c) $\tilde{z}_L = -2jz_0$
 $\tilde{h}_L = -j2$
 $\dots \tilde{\Gamma} \approx 1 \angle -53^\circ$

(d) $\tilde{z}_L = 0$
 $\tilde{h}_L = 0$
 $\tilde{\Gamma} = -1$

you should have this memorized by now!
 ☺

b) $\tilde{z}_L = (2 - 2j)z_0$
 $\tilde{h}_L = 2 - j2$
 $\dots \tilde{\Gamma} \approx 0.628 \angle 29.5^\circ$

(D)

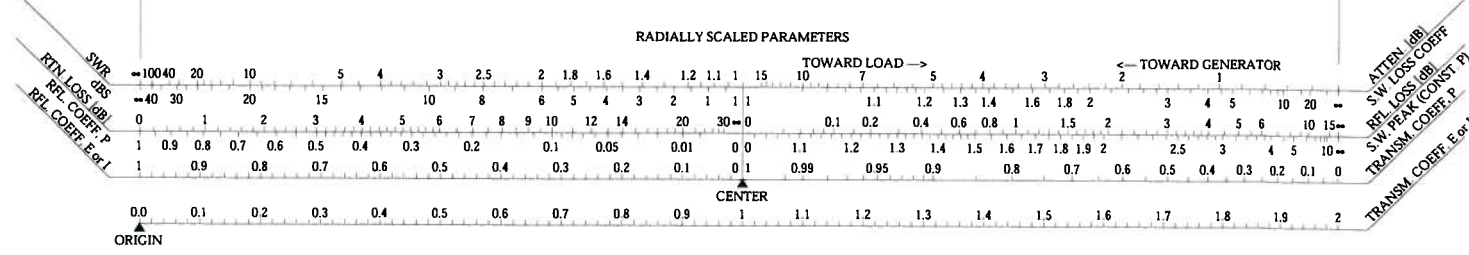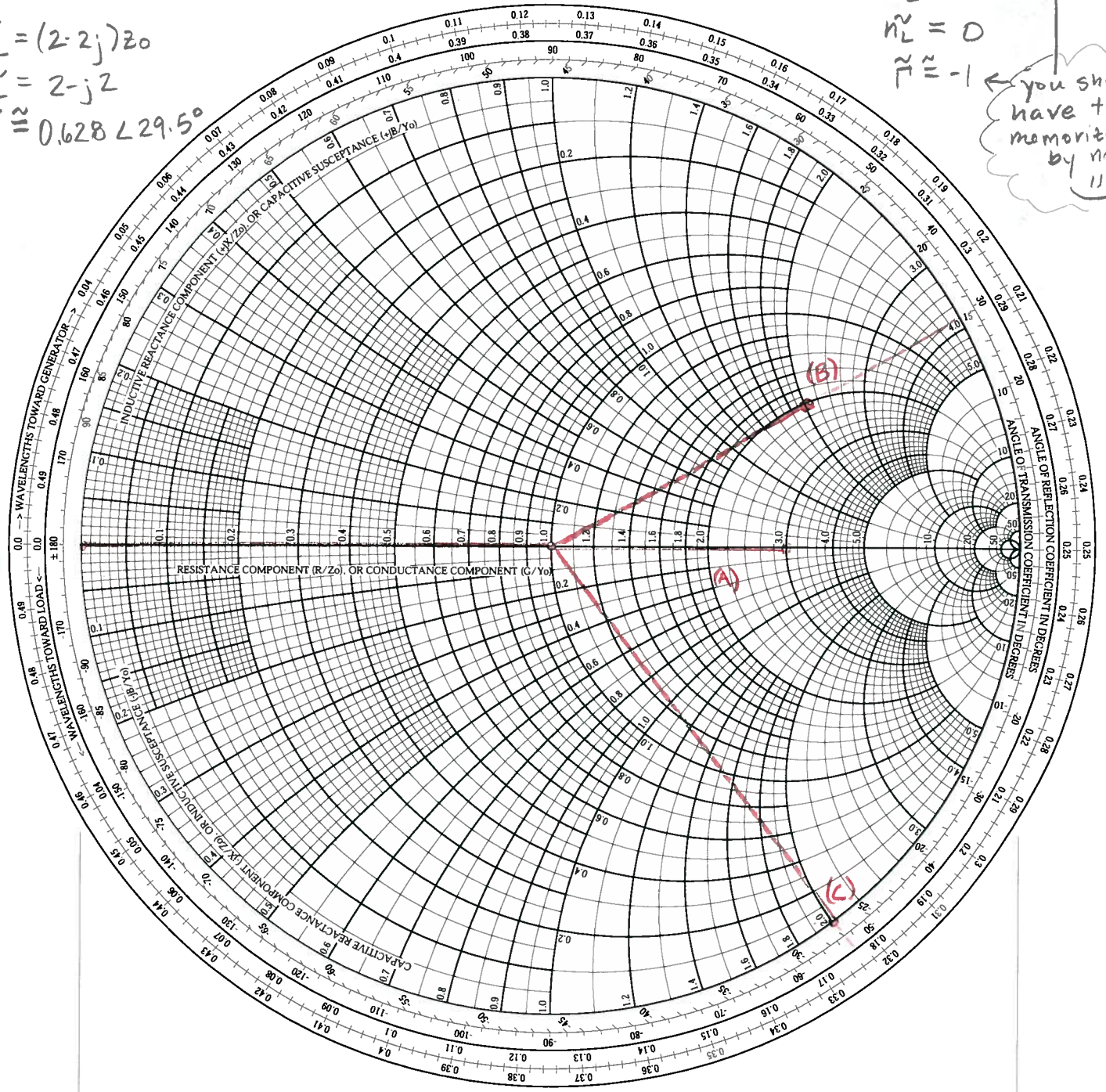

(2.36) (a) $\tilde{\Gamma} = 0.5$ $\tilde{n}_L = 3 + j0$

(b) $\tilde{\Gamma} = 0.5 \angle 60^\circ$ $\tilde{n}_L = 1.03 + j1.15$


(c) $\tilde{\Gamma} = -1$ $\tilde{n}_L = 0$ **The Complete Smith Chart**
Black Magic Design

(d) $\tilde{\Gamma} = 0.3 \angle -30^\circ$ $\tilde{n}_L = 1.6 - j0.52$

(e) $\tilde{\Gamma} = 0$
 $n_L = 1 + j0$

(f) $\tilde{\Gamma} = j$
 $n_L = 0 + j$

(c)

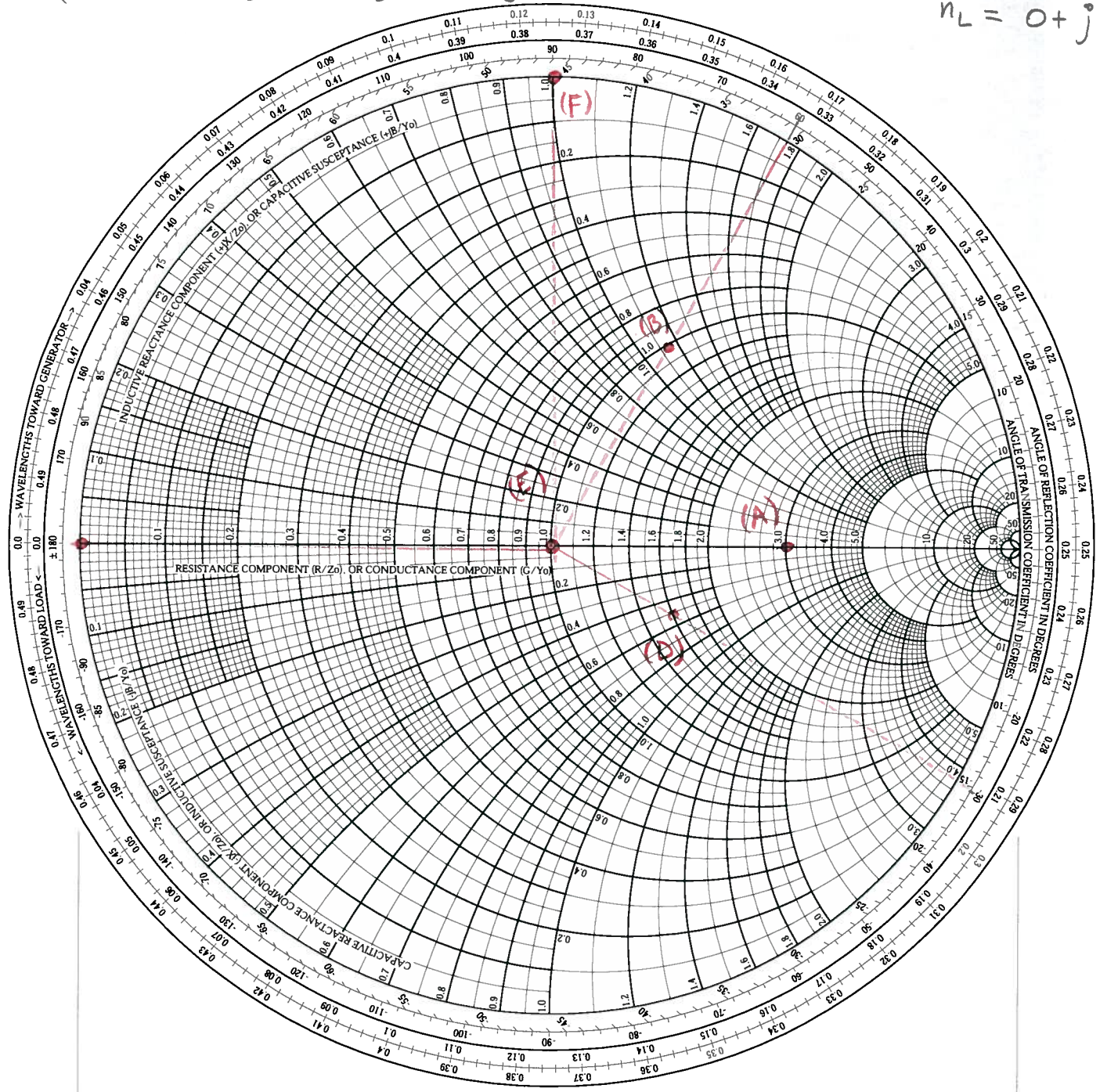

RADIALLY SCALED PARAMETERS

